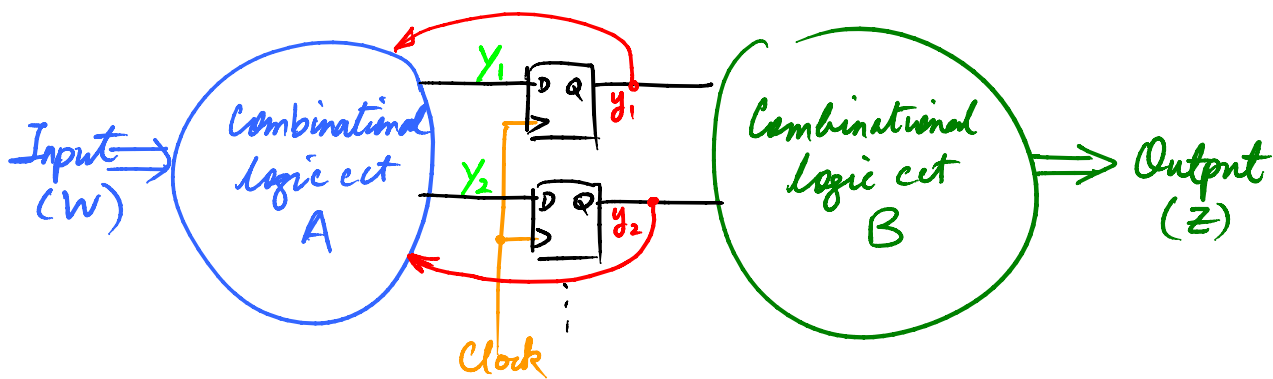


6.1-2 Finite State Machine (FSM) - moore model



A FSM is a sequential circuit that has inputs (W), finite states (Y) and outputs (Z).


present states at any given clock cycle are represented by y_1, y_2, \dots (Q 's of FF 's)

next states are represented by Y_1, Y_2, \dots (D 's of FF 's)

Design example = design a FSM that controls a machine which receives a status signal (W) and produce an output error signal (Z) when ever a pattern of "101" in three successive clock cycles has occurred. i.e. Z should be set to "1" in the next clock cycle and then set back to "0" afterward.

Clock cycle:	1	2	3	4	5	6	7	8	9	...
W :	0	0	1	1	0	1	0	1	1	...
Z :	0	0	0	0	0	0	1	0	1	...

By inspection

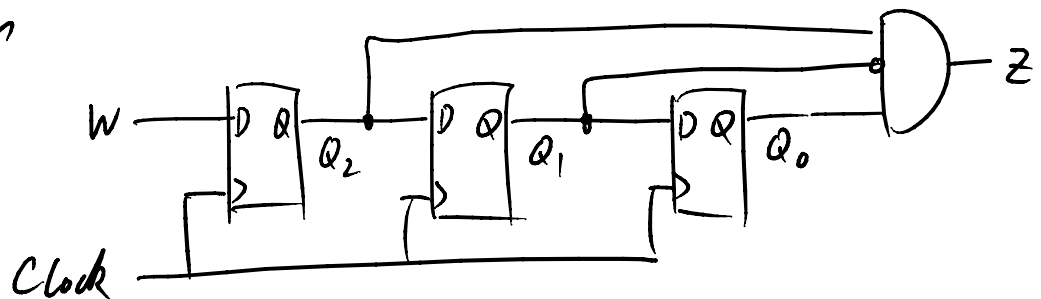


Design Procedure for FSM

1. Draw state diagram (from your understanding of the problem)
2. Draw State table (different form of the state diagram)
3. choose # of FFs to represent those states ($\geq \log_2(\text{\# of states})$)
4. Draw state-assigned table (use FFs to encode states)
5. Derive the combinational logic blocks A & B.
6. Draw the FSM circuit.

→ go back to our "101" pattern recognition problem.

1. State Diagram

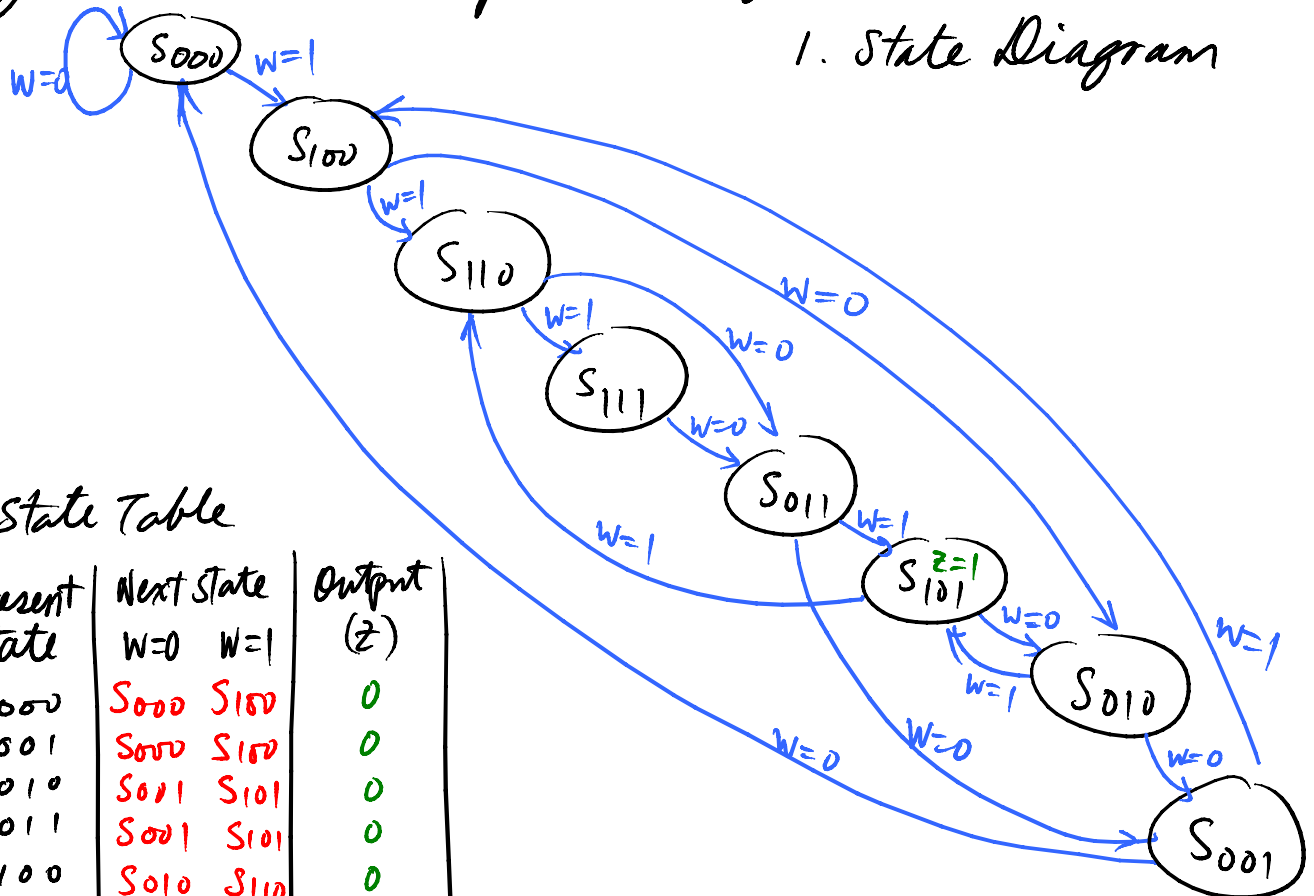

2. State Table

Present State	Next State		Output (z)
	W=0	W=1	
S000	S000	S100	0
S001	S000	S100	0
S010	S001	S101	0
S011	S001	S101	0
S100	S010	S110	0
S101	S010	S110	1
S110	S011	S111	0
S111	S011	S111	0

State names W - input

3. How many FFs are needed to represent 8 states? (3)


$$y_2 y_1 y_0 = 000 \text{ for } S_{000}$$

$$y_2 y_1 y_0 = 001 \text{ for } S_{001}$$

} state encoding
or state assignment

4. State-assigned Table

Present state $y_2 y_1 y_0$	Next State		Output z
	$W=0$ $y_2 y_1 y_0$	$W=1$ $y_2 y_1 y_0$	
0 0 0	0 0 0	1 0 0	0
0 0 1	0 0 0	1 0 0	0
0 1 0	0 0 1	1 0 1	0
0 1 1	0 0 1	1 0 1	0
1 0 0	0 1 0	1 1 0	0
1 0 1	0 1 0	1 1 0	1
1 1 0	0 1 1	1 1 1	0
1 1 1	0 1 1	1 1 1	0

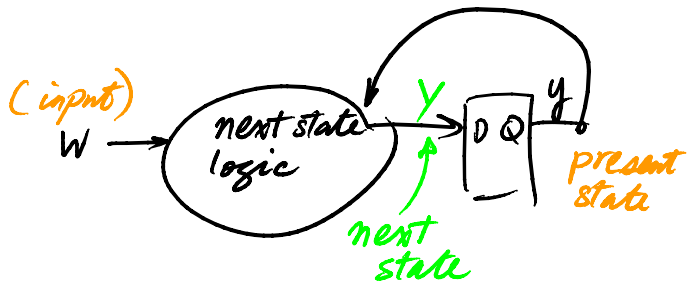

We want to find y_2 as a function of W (input) and $y_2 y_1 y_0$ (present state)

← K-map for y_2

$y_1 y_0$	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

by inspection

$$y_1 = y_2$$

$$y_0 = y_1$$

5. find next-state logic and output logic expression.

$$\text{output } z = y_2 \bar{y}_1 y_0$$

6. Draw the FSM circuit

