

Carry-ripple & Carry-lookahead adder

$$S_0 = x_0 \oplus y_0 \oplus C_0$$



$$C_1 = x_0 y_0 + x_0 C_0 + y_0 C_0$$

$$= x_0 y_0 + (x_0 + y_0) C_0$$

$$S_1 = x_1 \oplus y_1 \oplus C_1$$

$$C_2 = x_1 y_1 + (x_1 + y_1) C_1$$

} need to wait for C_1 signal

  

For a 16-bit adder: C_{16} ($16 \times 2 + 1 = 33$ gate delay)

Carry look-ahead adder (Fast adder)

$$S_0 = x_0 \oplus y_0 \oplus C_0$$

$$C_1 = x_0 y_0 + x_0 C_0 + y_0 C_0$$



$$= x_0 y_0 + (x_0 + y_0) C_0$$

} FA_0

$$\rightarrow g_0 + P_0 C_0$$

$$S_1 = x_1 \oplus y_1 \oplus C_1$$
  
$$C_2 = x_1 y_1 + (x_1 + y_1) C_1 = \overset{g_1}{x_1 y_1} + \overset{P_1}{(x_1 + y_1)} (\overset{g_0}{x_0 y_0} + \overset{P_0}{(x_0 + y_0) C_0}) = g_1 + P_1 g_0 + P_1 P_0 C_0$$



⇒ for 16 bit fast adder C_{16} (3 gate-level delay)


Pro's: fewer gate level delays

Con's: large number of inputs on gates.
fan-in

→ usually fan-in of 4 is acceptable.

What to do about a 16-bit adder?

 Option 1: Comb. of look-ahead and carry ripple





lookahead adder

$$C_4 = g_3 + P_3 C_3 = g_3 + \underbrace{P_3 g_2 + P_3 P_2 g_1 + P_3 P_2 P_1 g_0 + P_3 P_2 P_1 P_0 C_0}_{\text{product terms}}$$

- 1 gate level delay to generate g_i, P_i
- 1 gate level delay to generate all product terms
- 1 gate level delay to do the sum terms

Option 2: Hierarchical lookahead

  

$$* C_4 = G_0 + \underbrace{P_0 C_0}_{\substack{1 \text{ gate} \\ 1 \text{ gate}}}$$

$$C_8 = G_1 + P_1 C_4 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

where $G_1 = g_7 + P_7 g_6 + P_7 P_6 g_5 + P_7 P_6 P_5 g_4$ $\leftarrow +4 \text{ to index}$
 $P_1 = P_7 P_6 P_5 P_4$

gate-level delays = 5 for C_{16} .


quick contrasts: (C_{16}) gate-level delay

carry-ripple = 33


lookahead = 3 (large fan-in)

(opt 1) ripple-lookahead: 9 (fan-in ≤ 5)

 (opt 2) lookahead-lookahead: 5 (fan-in ≤ 5)




→ quick recall FA (Full Adder)

 

$$S_i = a_i \oplus b_i \oplus C_i$$


$$C_{i+1} = a_i b_i + (a_i + b_i) C_i$$

4-bit adder using the above FA.

 

Carry-bypass adder

 if a_i, b_i are different, $(1,0)$ or $(0,1)$, $C_4 = C_0$ (**)
for a larger adder (8 bits)



Q: What is the worst-case delay through the 8-bit adder?


A: look at the carry-bypass adder ①

case 1: when any one $a_i b_i$ pair have the same value.



C_8 is independent of C_4

 case 2: when all pairs $a_i b_i$ are different, i.e. $(1,0)$ or $(0,1)$.



$C_8 = C_4$
 bypass path (**)