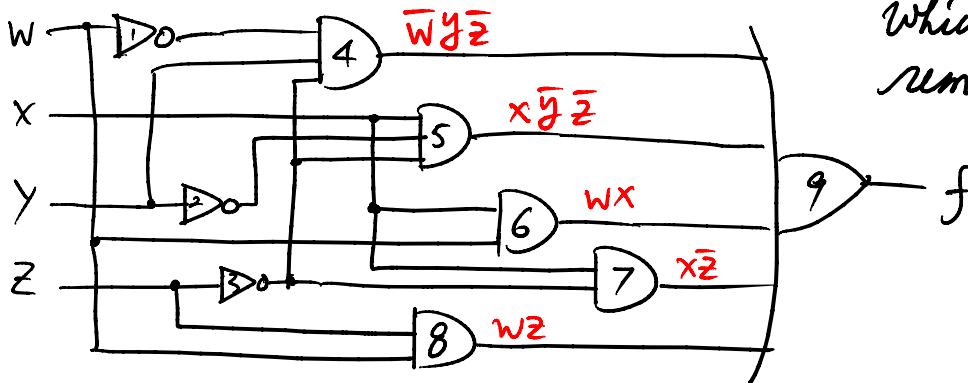


## 2012 Midterm


Q1. Boolean Algebra

$$\begin{aligned}
 i) f &= \bar{a}d + \underline{a}d + \bar{b}c\bar{d} + \underline{\bar{a}b\bar{c}\bar{d}} + \underline{a\bar{b}c\bar{d}} \\
 &= \underline{d} + \underline{\bar{b}c\bar{d}} + \underline{\bar{b}c\bar{d}} \quad (\text{combining}) \\
 &= \underline{d} + \underline{\bar{b}c} \quad (\text{combining})
 \end{aligned}$$

Q2.



Which gates can be removed?




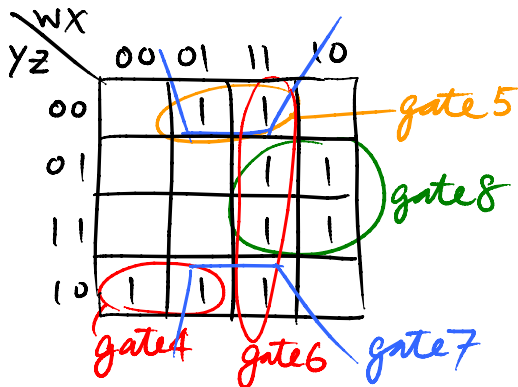


minimal SOP cover is


$$f = \underbrace{\bar{W}y\bar{z}}_{\text{gate 4}} + \underbrace{x\bar{z}}_{\text{gate 7}} + \underbrace{WZ}_{\text{gate 8}}$$

gates to remove = 2, 5 and 6

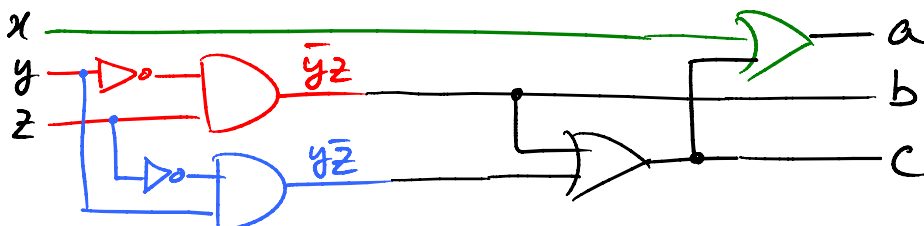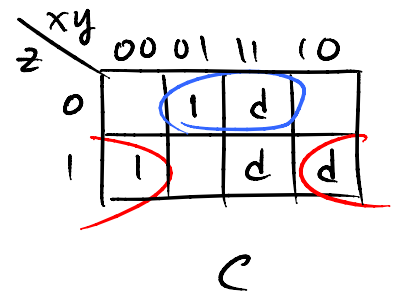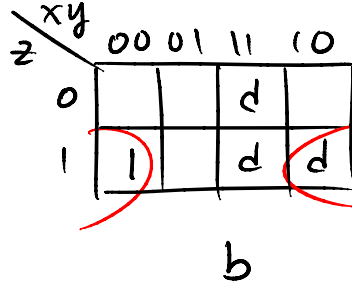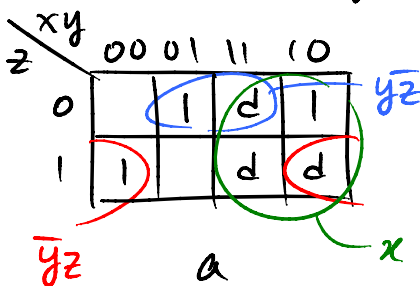
Q4. 7-seg. display, find SOP for a, b and c to achieve min. total cost



Q6. i)

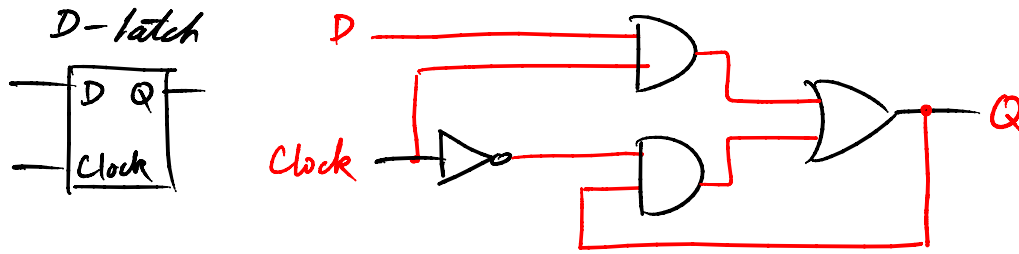

ii)

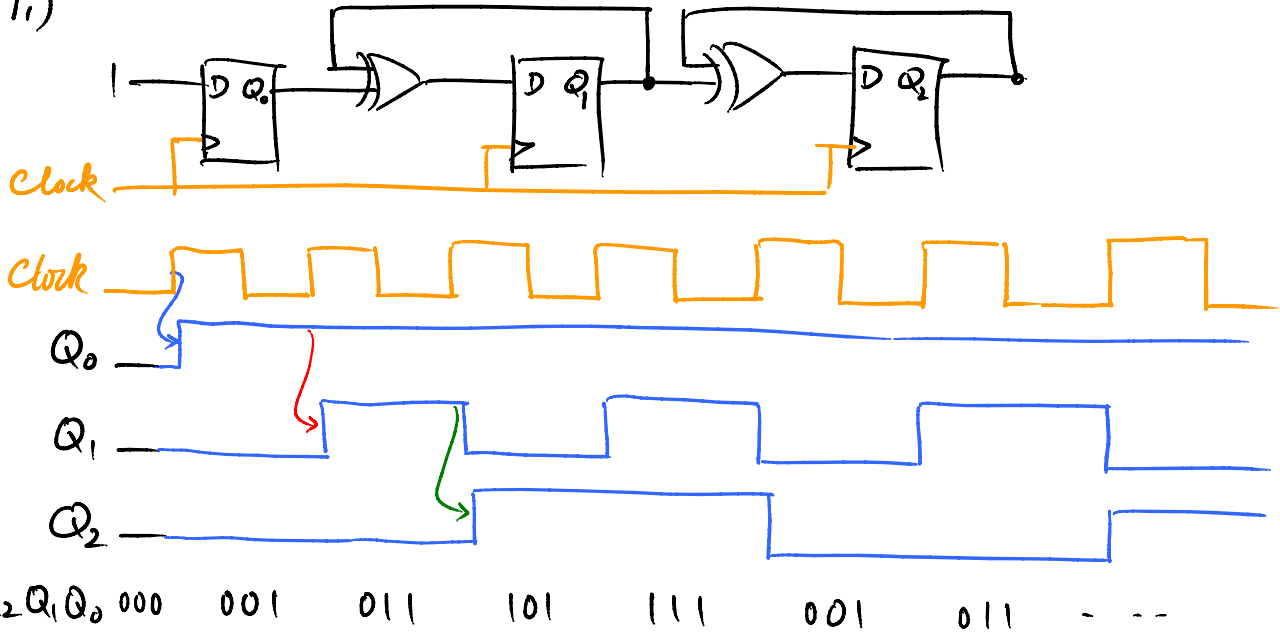


Q7. consider 3-bits input  $S_2 S_1 S_0$  and 3-bits output  $Z_2 Z_1 Z_0$ , for input numbers 0, 1, 2 or 3, outputs should get one greater than the input numbers. for the rest, outputs should get one less than the input numbers.

i) truth table


$S_2$	$S_1$	$S_0$	$Z_2$	$Z_1$	$Z_0$	
0	0	0	0	0	1	} $z = s + 1$
0	0	1	0	1	0	
0	1	0	0	1	0	
0	1	1	1	0	0	
1	0	0	0	1	0	} $z = s - 1$
1	0	1	1	0	0	
1	1	0	1	0	1	
1	1	1	1	1	0	

Q8 i)

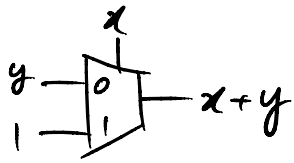

This is a 2 input OR gate

ii)

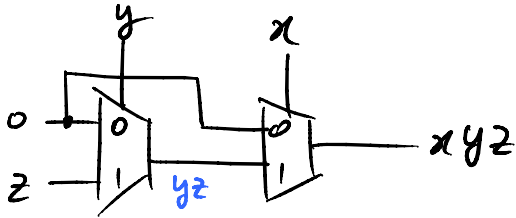

This is a 3-input AND gate