 


## Arithmetic Circuits (Adder, Subtractor)

Recall full adder (FA)



$C_i$	$b_i$	$a_i$	$C_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	0
1	1	1	1	1


\* using  $a_i$  would have the same effect.  
because this value goes through only when  
both  $a_i$  and  $b_i$  have the same value

## Verilog for a FA

```
module FA (input Cin, a, b, output Cout, S);
    assign  $S = Cin \wedge a \wedge b$ ;
    assign  $Cout = (a == b) ? b : Cin$ ;
endmodule
```

Conditional assignment

 Verilog code for n bit adder using  
a "for" loop



```
Module addn (Cin, A, B, Cout, S);
```

```
parameter n=4;
```

```
input Cin;
```

```
input [n-1:0] A, B;
```

```
output reg Cout;
```

```
output reg [n-1:0] S;
```

```
reg [0:n] C;
```

```
always@ (*);
```

```
begin
```

```
    C[0] = Cin; // initialization
```

```
    for (k=0; k<n; k=k+1)
```

```
    begin
```

```
         $S[k] = A[k] \wedge B[k] \wedge C[k]$ ;
```

```
         $C[k+1] = (A[k] == B[k]) ? A[k] : C[k]$ ;
```

```
    end
```

## Using the "+" operator


```
for (k=0; k<n; k=k+1)
```

```
{C[k+1], S[k]} = A[k] + B[k] + C[k];
```



$$\begin{array}{r} A(k) \\ B(k) \\ + C(k) \\ \hline C[k+1] \ S[k] \end{array}$$

$C_{out} = C[n];$   
end  
endmodule

 

module Addn (...);  
parameter n=4;  
...  
always @ (\*)  
{ Cout, S } = A + B + Cin;  
endmodule

## Signed Numbers (2's complement)

4-bit binary

to add  $5+1=6$

$$5+(-1)=4$$

$$5+(1111)=4$$

$$\left. \begin{array}{l} 5+(-1)=4 \\ 5+(1111)=4 \end{array} \right\} -1 \leftarrow 1111$$

$$5+(-2)=3$$

$$5+(1110)=3$$

$$\left. \begin{array}{l} 5+(-2)=3 \\ 5+(1110)=3 \end{array} \right\} -2 \leftarrow 1110$$

0	0	0	0	0	+4	
+1	0	0	0	1		+15
+2	0	0	1	0		
+3	0	0	1	1		
+4	0	1	0	0	+1	
+5	0	1	0	1		
+6	0	1	1	0		
+7	0	1	1	1		
-8	1	0	0	0	-1	
-7	1	0	0	1		
-6	1	0	1	0		
-5	1	0	1	1		
-4	1	1	0	0		
-3	1	1	0	1		
-2	1	1	1	0		
-1	1	1	1	1		

for 4 bits.

to represent  $-k$  we can do

$$\begin{array}{r} 2^4 - k \\ \hline 2^4 = (16)_{10} \\ \hline 16 \\ -1 \\ \hline 15 \end{array} \quad \text{eg. } -k = -1$$

$$2^4 = (10000)_2$$

for  $n$  bit.  $-k \leftarrow 2^n - k$

another way  $\leftarrow [(2^n - 1) - k] + 1$

$$\begin{array}{r} 1 \ 1 \ \dots \ 1 \ (2^n - 1) \\ - k_{n-1} \ k_{n-2} \ \dots \ k_0 \\ \hline \bar{k}_{n-1} \ \dots \ \bar{k}_0 \ (\bar{k}) \\ + 1 \\ \hline \text{2's comp. of } -k \end{array}$$


eg.  $n=4$ , we try to find  $-1$

$$2^n - 1 \rightarrow \begin{array}{cccc} 1 & 1 & 1 & 1 \end{array} \quad (2^4 - 1 = 15)$$

$$\begin{array}{cccc} - & 0 & 0 & 0 & 1 \end{array} \quad (1)$$

$$\begin{array}{cccc} 1 & 1 & 1 & 0 \end{array} \quad \leftarrow \text{complement of 1}$$
 
$$\begin{array}{cccc} + & & & 1 \\ \hline 1 & 1 & 1 & 1 \end{array} \quad (2's \text{ complement of } -1)$$



when  $\overline{Add/sub} = 0$   
it is  $A+B$

when  $\overline{Add/sub} = 1$   
it is  $A-B$

To find 2's complement of  $k$ , ① complement  $k \rightarrow \bar{k}$

eg. 4 bit system, if we want  $-6$ , ② then do  $\bar{k} + 1$

$$\begin{array}{r} 0110 \text{ (+6)} \\ 1001 \text{ (comp)} \end{array}$$

$$\begin{array}{r} ② \quad + \quad 1 \\ \hline 1010 \text{ (-6 in 2's comp)} \end{array}$$

Shortest cut to find the 2's complement

eg. 4 bit signed number

$$\begin{array}{r} 0110 \text{ (2's comp. of } -6) \\ \hline 1010 \end{array}$$

(4 bit +6)

complement the remaining bits

copy down all 0's and the 1st "1" you see from the right hand side (ie. starting from the lowest bit)


Multiplication  
(for +ve #s)

$$\begin{array}{r} (22)_{10} \\ \times (13)_{10} \\ \hline 66 \\ + 22 \\ \hline (286)_{10} \end{array} \quad \begin{array}{r} 12 \\ \times 11 \\ \hline 12 \\ + 12 \\ \hline 132 \end{array}$$


$$\begin{array}{r} 1100 \\ \times 1011 \\ \hline 1100 \\ 1100 \\ 0000 \\ + 1100 \\ \hline 10000100 \end{array}$$

$$\begin{array}{l} A = a_3 a_2 a_1 a_0 \\ \times B = b_3 b_2 b_1 b_0 \\ \hline P = P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0 \end{array}$$
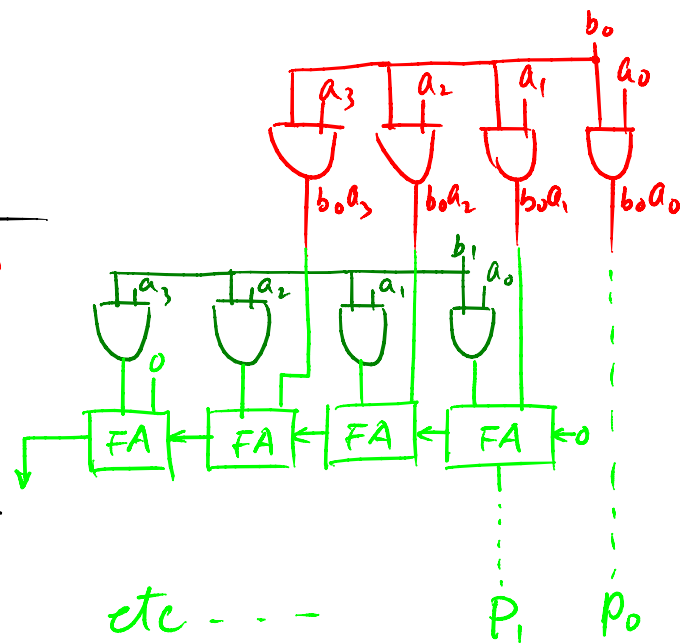
$$\begin{array}{r} a_3 \ a_2 \ a_1 \ a_0 \\ \times b_3 \ b_2 \ b_1 \ b_0 \\ \hline b_0 a_3 \ b_0 a_2 \ b_0 a_1 \ b_0 a_0 \\ b_1 a_3 \ b_1 a_2 \ b_1 a_1 \ b_1 a_0 \\ b_2 a_3 \ b_2 a_2 \ b_2 a_1 \ b_2 a_0 \\ +) b_3 a_3 \ b_3 a_2 \ b_3 a_1 \ b_3 a_0 \\ \hline P_7 \ P_6 \ P_5 \ P_4 \ P_3 \ P_2 \ P_1 \ P_0 \end{array}$$



Finite State Machine (FSM)

 

Digital  
Systems