
SRAM: Static Random Access Memory memory cell is	> -7
DRAM = Dynamic Random Access Memony memony cell looks like	- Capacit
Connection of SRAM chip to the FPGA (on	DE2 board)
→ each pin on our SRAM chip is connected to (Cyclone II 2c35). → each pin has a name like SRAM_DQ	
(in DE2-pin-assignment.gsf) SRAM-Address SRAM-WE-N, Data-rend (8) Address	
Data-write WE FSM \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \	
$\begin{array}{c c} Cyclme & \phi & \hline \\ 2C35 & \phi & \hline \end{array}$	
Describing Tri-state - in verilog	
inout [15:0] SRAM_DQ;	meuns tri-state

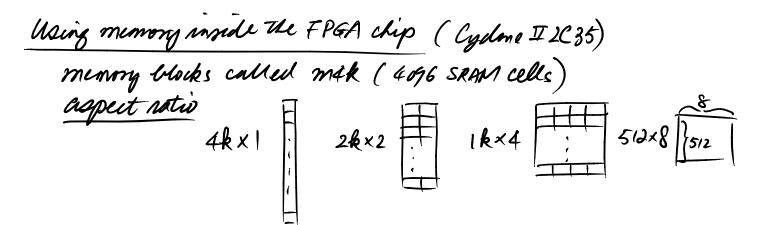
assign Data-read = SRAM_DQ; assign SRAM-DQ = (SRAM_NE_N == 0?) Data-write: 16'bZ;




from Quartus I, use megawizard plug-in manager. select memory compiler


SRAM on DE2 brand (2 major differences)

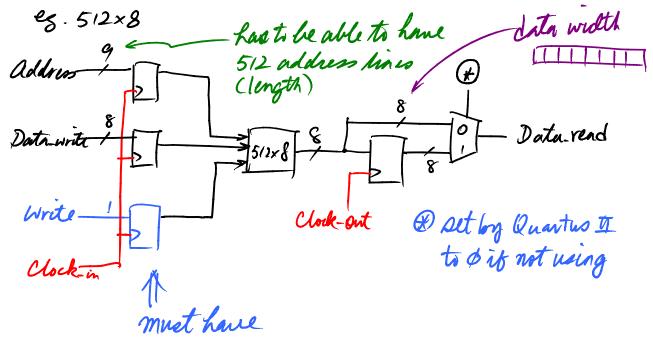- 1. Data In and Ostasut are separate vives (mo tri-state needed)
- 2. Addres, OutaIn, and write are all strand in registers (7+5) inseale the mak block.



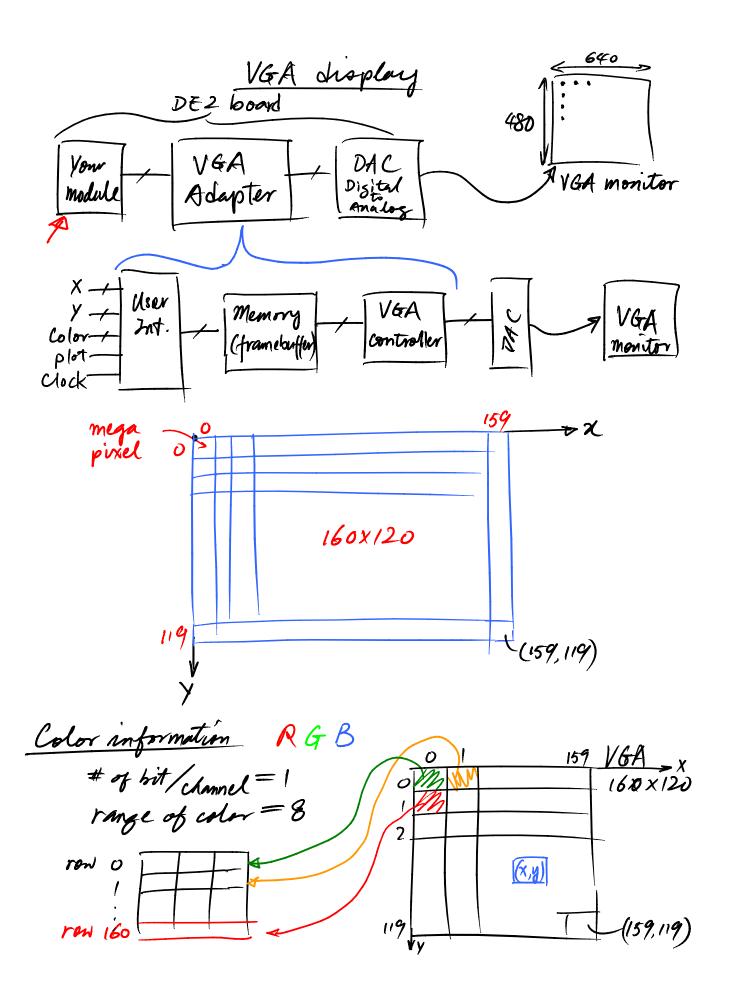

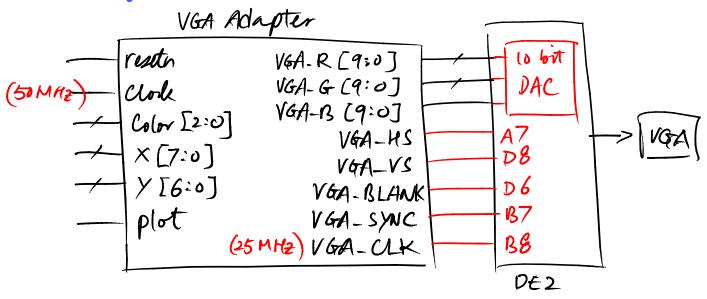Color information at coordinate (x, y) will be street in memory row = 160Y + X



Changing VOA adapter Parameters

Option One by instantiate

vga-adapter VGA (--
your name

| default 320×240" ="160×120" ;

defparam VGA. RESOLUTION = "160 x 120"; VGA. MONOCHROME = "FALSE";

VGA. COLOUR_CHANNEL_DEPTH = 1;

VGA. BACKGROUNDIMAGE = "image. colour.mif", default "background.mif"

Option two Schematic diagram

Vga_adapter. bsf Paramete

0178 020 CN 8

Value
1
"FALSE"
" 160×120"
"image colour mif"

Resources = bmp2mif-exe make it 160x 120 bmp2 mif your bmpfile = image colour met image. mono mif Shannon's Expansion Therem

> Implementing logic functions in multiplexers

