 


6.2, 6.8 FSM (cond.)

Let's work on the same "101" pattern detection problem from last lecture. (2nd version)

1. State Diagram



→ This design allows overlapping

State

A - waiting for "1"

B - seeing first "1" in the pattern

C - seeing "1" followed by "0"

D - seeing "101" pattern

2. State Table

| P.S | N.S | | Output z |
|-----|-----|-----|-------------|
| | w=0 | w=1 | |
| A | A | B | 0 |
| B | C | B | 0 |
| C | A | D | 0 |
| D | C | B | 1 |

3. 2 FF's $y_2 y_1 = 00$ (A), $y_2 y_1 = 01$ (B), $y_2 y_1 = 10$ (C), $y_2 y_1 = 11$ (D)

State-assigned table

| P.S. | N.S | | Output z |
|-----------|-----------|-----------|-------------|
| | w=0 | w=1 | |
| $y_2 y_1$ | $y_2 y_1$ | $y_2 y_1$ | |
| (A) 00 | 00 | 01 | 0 |
| (B) 01 | 10 | 01 | 0 |
| (C) 10 | 00 | 11 | 0 |
| (D) 11 | 10 | 01 | 1 |



4. Next-state and output expressions

| w \ $y_2 y_1$ | 00 | 01 | 11 | 10 |
|---------------|----|----|----|----|
| 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

$$y_2 = y_1 \bar{w} + y_2 y_1 w$$

$$y_1 = w \text{ (by inspection)}$$


$$z = y_2 y_1$$

  

Verilog code for a FSM can be written by using 3 blocks:
 combinational circuit A, FFs, combinational circuit B


```
module seq01 (input clock, W, Resetn, output Z);
  reg [2:1] y, Y; // y2, y1 are the present states, Y2, Y1 are the next states
  parameter A=2'b00, B=2'b01, C=2'b10, D=2'b11; // state assignment
  // combinational circuit A, describing state transitions
```
 
```
  always@(w, y)
    case (y)
      A: if (!w) Y=A;
          else Y=B;
      B: if (!w) Y=C;
          else Y=B;
      C: if (!w) Y=A;
          else Y=D;
      D: if (!w) Y=C;
          else Y=B;
    endcase
```



```
  // FFs describing D-ff's with synchronous reset
  always@(posedge clock)
```
 
```
    if (Resetn == 0)
      y <= A;
    else
      y <= Y;
```




```
  // combinational circuit B, describing output logic
  assign Z = (y == D); // z=1 if P.S is D
```

```
endmodule
```

⇒ Another style of state encoding → One-hot encoding
 let's work on the same "101" pattern detection example

State diagram

 

Use 4 FFs to represent this design

$y_4 y_3 y_2 y_1 =$

| | | | | |
|---|---|---|---|-----|
| 0 | 0 | 0 | 1 | (A) |
| 0 | 0 | 1 | 0 | (B) |
| 0 | 1 | 0 | 0 | (C) |
| 1 | 0 | 0 | 0 | (D) |

Describe next-state logic.

$$Y_1 = y_1 \bar{w} + y_3 \bar{w} = (y_1 + y_3) \bar{w}$$

↑ gives you current state
 ↑ gives you input value

$$Y_2 = y_1 w + y_2 w + y_4 w = (y_1 + y_2 + y_4) w$$

$$Y_3 = y_2 \bar{w} + y_4 \bar{w} = (y_2 + y_4) \bar{w}$$

$$Y_4 = y_3 w$$

Output logic $z = y_4$

Design example (Arbiter) — design a FSM that controls access to a shared resource by three devices. Each device requests use of the resource by asserting r_1, r_2 or r_3 . The Arbiter decides which device "gets" the resource, and sets its grant signal g_1, g_2 or g_3 . There is a priority scheme = $r_1 > r_2 > r_3$.

