 


# Electronic Memory

— All memory units consists of two parts =

1. decoder
2. array of memory cells



Decoder: a ckt. of inputs ( $m$ ) and  $2^m$  outputs. which uses one-hot encoding. ex for  $m=3$

$A_2$	$A_1$	$A_0$	$O_7$	$O_6$	$O_5$	$O_4$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

for a typical comp. processor, # of address lines = 32. the total rows addressable is  $2^{32} = 4,294,967,296$  (4 G)

## Memory cell array


— based on two basic concepts

- ① storage cells (feedback loop)
- ② tri-state (logic values: 0, 1, Z)




$E$	in	out
0	X	Z (no conn. action)
1	0	0
1	1	1

## tri-state in action

 

if  $WE = 1$ , allows us to store data on Data-write into the Storage cell.

 
if  $WE = 0$ , allows us to read the data from the storage cell through Data-read.



$O_i$  - output of the decoder


(\*) this "weaker" inverter allows for data to be written into the storage cell (ie allows data to change  $1 \rightarrow 0$  or  $0 \rightarrow 1$ )

## Array of memory cells

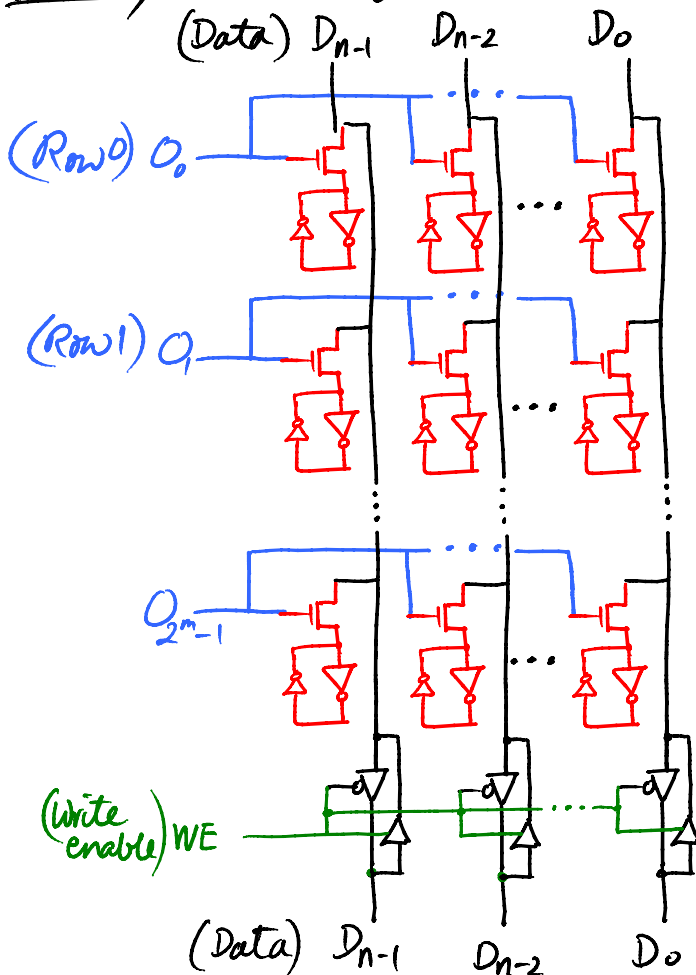


Q: why would we need the tri-state buffers on the data outputs?

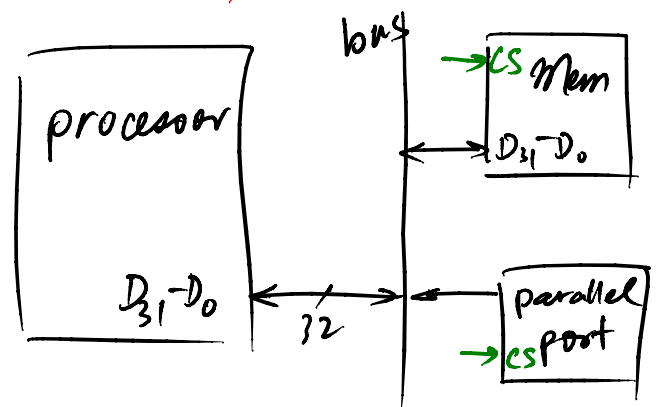A: In an application, such as a computer, the memory chip is just one of several chips that have to share the data wires (bus)




cs - chip select.

example: memory chip 1561LV25616  
A2-10

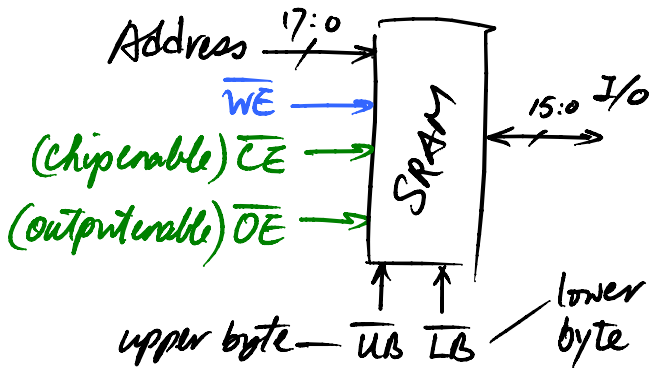

— To use the chip, we need to obey the timing requirements

 
To read a row of data  $\overline{CE} = \overline{OE} = 0, \overline{WE} = 1$



$t_{AA}$  — address access time (10ns)

$t_{OHA}$  — output hold address

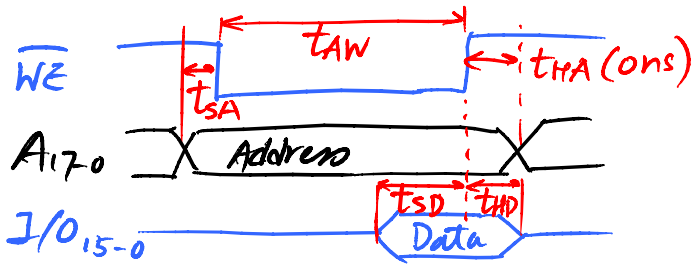To write a row of data ( $\overline{CE} = 0$ )



$t_{SA}$  — setup address time (0ns)

$t_{AW}$  — address width time (8ns)

$t_{SD}$  — setup data time (6ns)

$t_{HD}$  — hold data time (0ns)