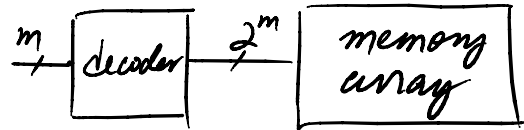


4.2, 3.5 Arithmetic Circuits



→ Decoder = 7-segment decoder



memory address (one-hot) decoder



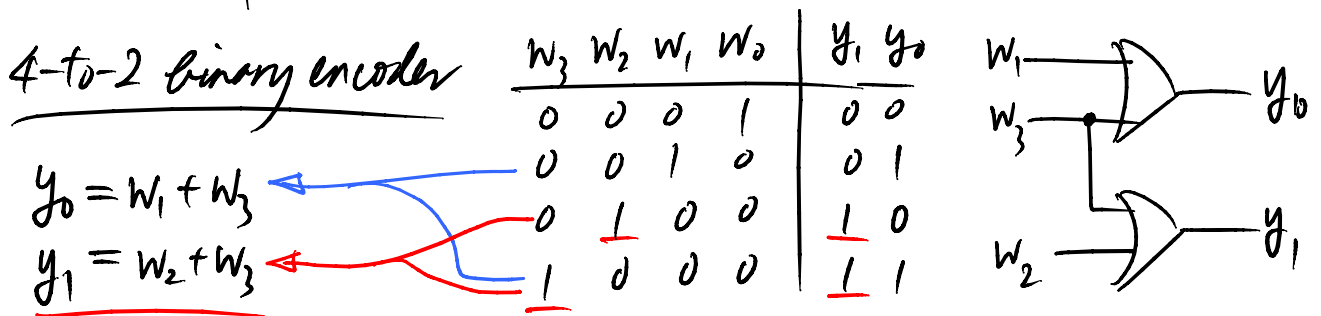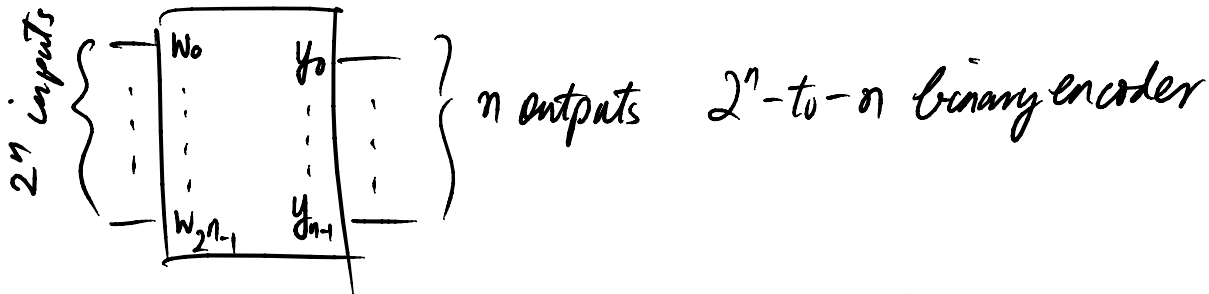→ Encoder = performs the opposite function of a decoder used to reduce the number of bits needed to represent some given information



→ Priority encoder order ($w_3 > w_2 > w_1 > w_0$)

	w_3	w_2	w_1	w_0	y_1	y_0	z
	0	0	0	0	d	d	0
$i_0 \rightarrow$	0	0	0	1	0	0	1
$i_1 \rightarrow$	0	0	1	d	0	1	1
$i_2 \rightarrow$	0	1	d	d	1	0	1
$i_3 \rightarrow$	1	d	d	d	1	1	1
					\uparrow	\uparrow	

← indicates if any input has been set

intermediate functions

$$i'_0 = \overline{w_3} \overline{w_2} \overline{w_1} w_0$$

$$i'_1 = \overline{w_3} \overline{w_2} w_1$$

$$i'_2 = \overline{w_3} w_2$$

$$i'_3 = w_3$$

$$y_1 = i'_2 + i'_3$$

$$y_0 = i'_1 + i'_3$$


$$z = i'_0 + i'_1 + i'_2 + i'_3$$

Comparator Circuit


Two 3-bit numbers $A = a_2 a_1 a_0$ and $B = b_2 b_1 b_0$

How to compare A and B? $\Rightarrow A \leq B$, $A > B$, $A \neq B$

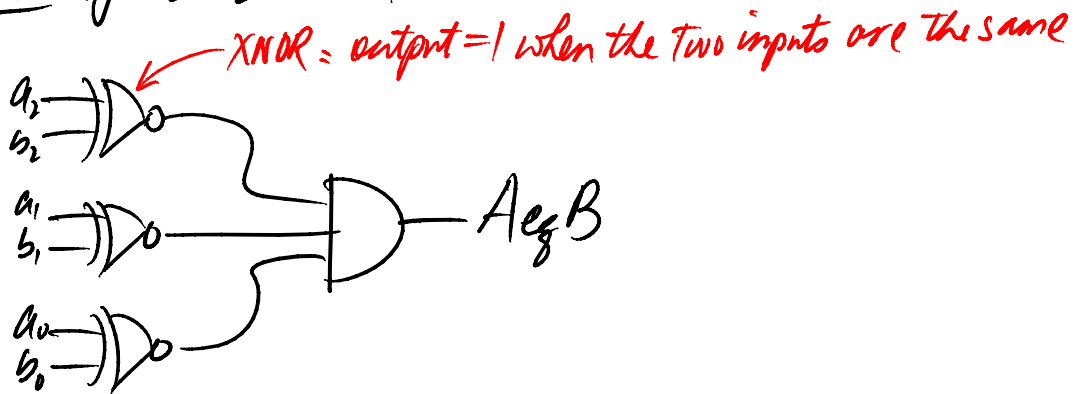
$A \leq B$ if $a_2 = b_2$ and $a_1 = b_1$ and $a_0 = b_0$



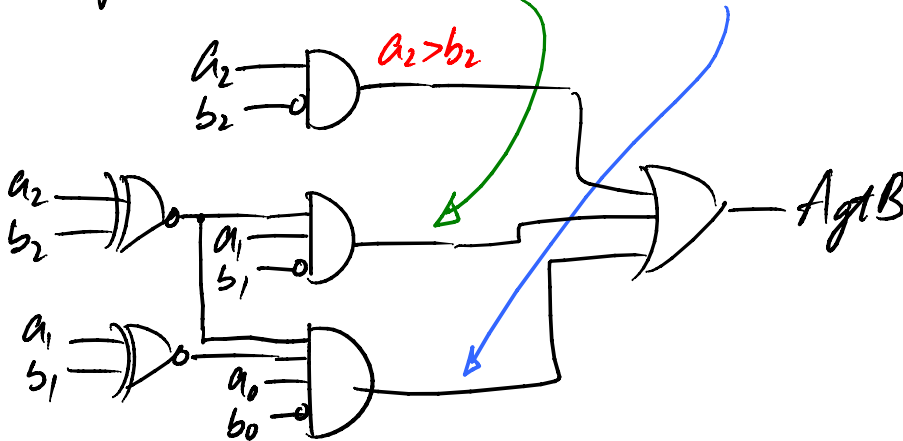$A > B$ if $a_2 > b_2$ OR $a_2 = b_2$ and $a_1 > b_1$ OR $a_2 = b_2$ and $a_1 = b_1$ and $a_0 > b_0$



$A \neq B$ $\overline{A \leq B + A > B}$

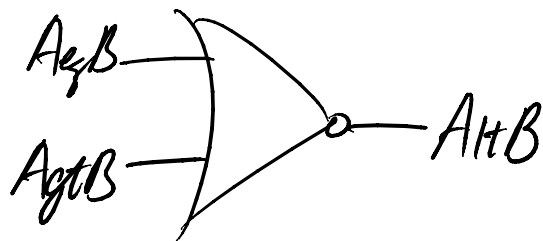

3.6 Multiplication Circuit

(let's use positive numbers)

$$\begin{array}{r}
 12 \\
 \times 11 \\
 \hline
 12 \\
 + 12 \\
 \hline
 132
 \end{array}
 \qquad
 \begin{array}{r}
 1100 \\
 \times 1011 \\
 \hline
 1100 \leftarrow \\
 1100 \leftarrow \\
 0000 \leftarrow \\
 + 1100 \leftarrow \\
 \hline
 10000 \mid 00
 \end{array}$$

multiply by 1

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \\
 \times b_3 \ b_2 \ b_1 \ b_0 \\
 \hline
 b_0 a_3 \ b_0 a_2 \ b_0 a_1 \ b_0 a_0 \text{ (row 1)} \\
 b_1 a_3 \ b_1 a_2 \ b_1 a_1 \ b_1 a_0 \text{ (row 2)} \\
 b_2 a_3 \ b_2 a_2 \ b_2 a_1 \ b_2 a_0 \\
 +) b_3 a_3 \ b_3 a_2 \ b_3 a_1 \ b_3 a_0 \\
 \hline
 p_7 \ p_6 \ p_5 \ p_4 \ p_3 \ p_2 \ p_1 \ p_0
 \end{array}$$

