 




B6.5 FPGA (Field programmable gated array)




Each LE can store a truth table that represents the logic function that is implemented. i.e. If the LE has k inputs, then it can represent any k -input logic function

eg. $k=2$

x_1	x_2	f
0	0	0/1
0	1	0/1
1	0	0/1
1	1	0/1

  

x_1	x_2	f
0	0	1
0	1	1
1	0	0
1	1	0

 

← called Look-up table (LUT)

on DE2, there 35,000 4-input LUTs.

3.2 Ripple-carry adder

recall adding 2 bits =

$$\begin{array}{r} x \\ + y \\ \hline c \quad s \end{array}$$

x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$c = xy$$



$$s = \bar{x}y + x\bar{y}$$

3-input XOR

x	y	z	XOR
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

detecting "odd" number of inputs being "1"

$$XOR = x \oplus y \oplus z$$

  

Verilog \wedge

extend to adding multi-bits: $A = a_2 a_1 a_0$ and $B = b_2 b_1 b_0$

eg. $A = 010$, $B = 111$

$$\begin{array}{r} \text{1100} \quad C_3 \ C_2 \ C_1 \ C_0 \\ (A) \ 010 \quad a_2 \ a_1 \ a_0 \\ (B) + 111 \quad b_2 \ b_1 \ b_0 \\ \hline 1001 \quad C_3 \ S_2 \ S_1 \ S_0 \end{array}$$



C_i	b_i	a_i	C_{i+1}	S_i	
0	0	0	0	0	
0	0	1	0	1	←
0	1	0	0	1	←
0	1	1	1	0	←
1	0	0	0	1	←
1	0	1	1	0	←
1	1	0	1	0	←
1	1	1	1	1	←

$$\begin{array}{r} C_{i+1} \ C_i \\ a_i \\ +) \ b_i \\ \hline C_{i+1} \ S_i \end{array}$$

simplified logic expressions

$$S_i = a_i \oplus b_i \oplus C_i$$
  
$$C_{i+1} = \bar{C}_i b_i a_i + C_i \bar{b}_i a_i + C_i b_i \bar{a}_i + C_i b_i a_i = \underline{b_i a_i} + \underline{C_i a_i} + \underline{C_i b_i}$$



```
module Carry-Adder(A, B, Cin, S, Cout);
    input [2:0] A, B;
    input Cin;
    output [2:0] S;
    output Cout;
    wire C1, C2; // internal connections
    FA Bit0 (A[0], B[0], Cin, S[0], C1);
    FA Bit1 (A[1], B[1], C1, S[1], C2);
    FA Bit2 (A[2], B[2], C2, S[2], Cout);
endmodule
```

```
module FA(input a, b, Cin, output s, Cout);
    assign s = a ^ b ^ Cin; // XOR gate (⊕)
    assign Cout = (a & b) | (a & Cin) | (b & Cin);
endmodule
```

Verilog: procedural statement "Always" block

Recall 2-to-1 mux



```
module 2to1mux (input x1, x2, s, output f);  
    assign f = (~s & x1) | (s & x2);  
endmodule
```

alternative Verilog code for 2-to-1 mux (using if-else)

```
reg f;  
always@(x1, x2, s) *3  
{  
    if (!s) *2  
        f = x1;  
    else  
        f = x2;  
endmodule
```

→ $f = x1;$
if (s == 1)
f = x2;

*1 any signal assigned a value inside a "always" block must be declared as **reg**

*2 "if-else" statements must be inside a "always" block

*3 sensitivity list = variables that will affect the assigned signal, alternative notation

always@(*) ← all input signals

*4 if more statements are used inside the "always" block, you need to use

```
always@(*)  
begin  
    ;  
end
```

note: if-else is treated as a single statement

"Case" statement
→ must be used inside
a "always" block

case (s)

1'b0: f = x1;

1'b1: f = x2;

endcase

← cover all remaining cases.
default: ---