 



5.3-4 Gated D-latch



Gated RS latch			
CK	S	R	$Q(t+1)$
0	x	x	$Q(t)$
1	0	0	$Q(t)$
1	0	1	1
1	1	0	0
1	1	1	don't use


Gated D-latch		
CK	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

Timing Diagram

 


Q follows D when $CK=1$

Q holds the old value when $CK=0$

 

consider

 


A	B	f
0	x	0/1 hold old value (storage)
1	0	0
1	1	1

f follows B

Gated D-latch

Cascading 2 D-latches

 


Case 1: $CK=0$, $Q_m=D$, $Q=Q_{old}$

Case 2: $CK=1$, Q_m can't change, $Q=Q_m$


change takes place only at the eve edge of the CK

Timing Diagram

 

+ve edge triggered D-ff


edge sensitive

 

-ve edge triggered D-ff

latch is level sensitive

Verilog code for storage elements

 

Gated D-latch

```
module D-latch(input D, CLK, output Q);
```

```
  reg Q;
```


```
  always@(D, CLK)
```

```
    if (CLK == 1)
```

```
      Q = D;
```

```
endmodule
```

 it implies if CLK=0, don't make any change



+ve edge triggered D-flip flop

```
module D-ff (input D, CLK, output Q);
```

```
  reg Q;
```

```
  always@(posedge CLK)
```


```
    Q <= D;
```

```
endmodule
```


<= non-block statement,

What can you do with a D-ff?

→ use it as a storage (register)

 


1 bit register

 


2-bit register

Data to be store

 

Data stored in Q when Clock


→ use them as a shift register

 

eg. $w = 1001$

Clock	Q_2	Q_1	Q_0
t_1	1		
t_2	0	1	
t_3	0	0	1
t_4	1	0	0
t_5		1	0
t_6			1

→ shift register w/ parallel load

 

Blocking (=) / non-block (<=) statements

module nonBlocking(input w, clock, output Q1, Q2); (2-bit shift register)

reg Q1, Q2;

always@ (posedge clock)


begin

Q1 <= w;

Q2 <= Q1;

end

endmodule

 

module Blocking(input w, clock, output Q1, Q2);

reg Q1, Q2;

always@ (posedge clock)


begin

Q1 = w;

Q2 = Q1;

end



endmodule

 

* use non-blocking statements in f-f.

use blocking statements for combinational logic.

extending the master-slave D-flip-flop

  

Resetr → active low make output ($Q=0$)

$Resetr=0$, if clock=0, $C=1$, $Q=0$ (reset)

if clock=1, $B=1$, $A=1$, $C=1$, $Q=0$ (reset)

This is called active low asynchronous reset!

Setn → active low asynchronous set (or preset) $\Rightarrow Q=1$

There are different variations



```
module Dff (input D, clock, Resetn, output Q);
    reg Q;
    always@ (negedge Resetn, posedge clock)
        if (Resetn == 0)
            Q <= 0;
        else
            Q <= D;
endmodule
```

Resetn inside a sensitivity list means this is an asynchronous reset!

What about Synchronous Reset?

```
module Dff (input D, clock, Resetn, output Q);
    reg Q;
    always@ (posedge clock)
        if (!Resetn)
            Q <= 0;
        else
            Q <= D;
endmodule
```

to reset Q,
first set resetn=0
the change ($Q=0$)
will take place at
the next clock

a possible circuit to implement a Synchronous reset

