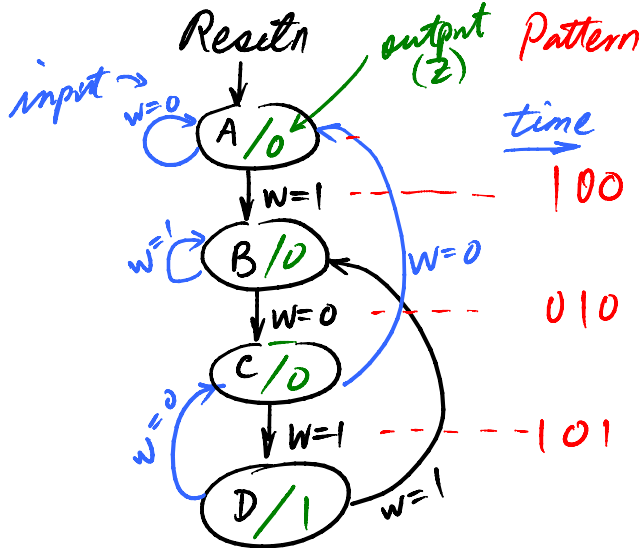


FSM (cond.)

Design example = "101" pattern recognition

1. State Diagram (2nd version)



meaning of each state

- A ← seeing "0" only
- B ← seeing 1st "1" in pattern
- C ← seeing "10" in pattern
- D ← seeing "101" in pattern


2. State Table

Present State	Next state		output z
	w=0	w=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

3. # of FFs = use $y_2 y_1 = 00$ (A), 01 (B), 10 (C), 11 (D)

P.S $y_2 y_1$	N.S		output z
	w=0 $y_2 y_1$	w=1 $y_2 y_1$	
0 0	0 0	0 1	0
0 1	1 0	0 1	0
1 0	0 0	1 1	0
1 1	1 0	0 1	1

4. Derive Comb. ckt A & B.


 


$$y_2 = y_1 \bar{w} + y_2 \bar{y}_1 w$$

$$y_1 = w$$

$$z = y_2 y_1$$

5. Draw FSM ckt.

  

— Verilog code for a FSM can be written by using three blocks:
Comb. ckt A, FFs, Comb. ckt B.

```
Module seq101 (input Clock, w, Resetn, output z);  
  reg [2:1] y, Y; // y2, y1 are the FFs present state  
                  // Y2, Y1 are the next state.
```

```
  parameter A=2'b00, B=2'b01, C=2'b10, D=2'b11;
```

```
  // Comb. ckt A describing state transitions
```

```
  always@ (w, y)
```

```
  case (y)
```

```
    A: if (!w) Y=A; (if input w=0, stay in state A)  
        else Y=B; (if input w=1, transition to state B)
```

```
    B: if (!w) Y=C;  
        else Y=B;
```

```
    C: if (!w) Y=A;  
        else Y=D;
```

```
    D: if (!w) Y=C;  
        else Y=B;
```

```
  end case
```

```
  // FFs
```

```
  always@ (posedge Clock)
```

```
    if (Resetn == 0) {
```

```
      y <= A;
```

```
    } // synchronous reset
```


```
    else
```

```
      y <= Y;
```

```
  // Comb. ckt B
```

```
  assign z = (y == D); { assign 1 to z if it's in state D
```

```
end module
```

 

Now, we can redo step 3 (choose # of FFs = 4)
(one FF for each state)

$$\begin{array}{l} y_4 y_3 y_2 y_1 = 0001 (A) \\ \quad \quad \quad 0010 (B) \\ \quad \quad \quad 0100 (C) \\ \quad \quad \quad 1000 (D) \end{array} \left. \vphantom{\begin{array}{l} y_4 y_3 y_2 y_1 = 0001 (A) \\ \quad \quad \quad 0010 (B) \\ \quad \quad \quad 0100 (C) \\ \quad \quad \quad 1000 (D) \end{array}} \right\} \begin{array}{l} \text{one-hot} \\ \text{state coding} \end{array}$$

consider all links pointing into A
(state transition into A)

1. when you are in state A and $w=0$
2. when you are in state C and $w=0$

$$Y_1 = \underset{\textcircled{1}}{y_1 \bar{w}} + \underset{\textcircled{2}}{y_3 \bar{w}} = (y_1 + y_3) \bar{w}$$

let's do it for state B

$$Y_2 = y_1 w + y_2 w + y_4 w = (y_1 + y_2 + y_4) w$$

for state C \longrightarrow

$$Y_3 = y_2 \bar{w} + y_4 \bar{w} = (y_2 + y_4) \bar{w}$$

for state D \longrightarrow


$$Y_4 = y_3 w$$

for output $z = y_4$ ($z=1$ whenever you are in state D)

Design example (Arbiter)

— design a FSM that controls access to a shared resource by three devices. Each device requests use of the resource by asserting r_1 , r_2 or r_3 . The arbiter decides which device "gets" the resource, and sets its grant signal g_1 , g_2 or g_3 . There is a priority scheme: $r_1 > r_2 > r_3$.

1. State Diagram

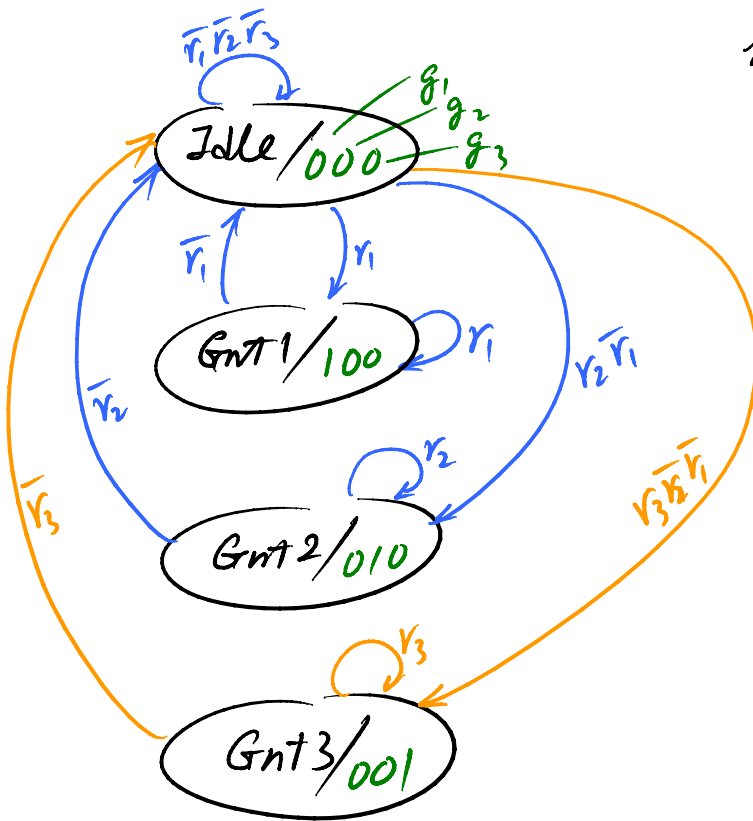

not necessary here, but
needed when some unusual
states exist.

2. use 2 FFs

```

Module arbiter(input R[1:3],
  input Clock, Resetn, output [1:3]G);
  reg [2:1] y, Y;
  parameter Idle = 2'b00, Gnt1 = 2'b01,
    Gnt2 = 2'b10, Gnt3 = 2'b11;
  
```

// State Diagram

always@ (y, R)

case (y)

Idle: if (R[1]) Y = Gnt1;
 else if (R[2]) Y = Gnt2;
 else if (R[3]) Y = Gnt3;
 else Y = Idle;

Gnt1: if (R[1]) Y = Gnt1;
 else Y = Idle;

Gnt2: if (R[2]) Y = Gnt2;
 else Y = Idle;

Gnt3: if (R[3]) Y = Gnt3;
 else Y = Idle;

Default: if (R[3]) Y = Gnt3;
 else Y = Idle;

// FFs

always@ (posedge Clock)

if (!Resetn) Y <= Idle;
 else Y <= Y;

// outputs

assign G[1] = (y == Gnt1);
 assign G[2] = (y == Gnt2);
 assign G[3] = (y == Gnt3);

end module

synchronous
reset