
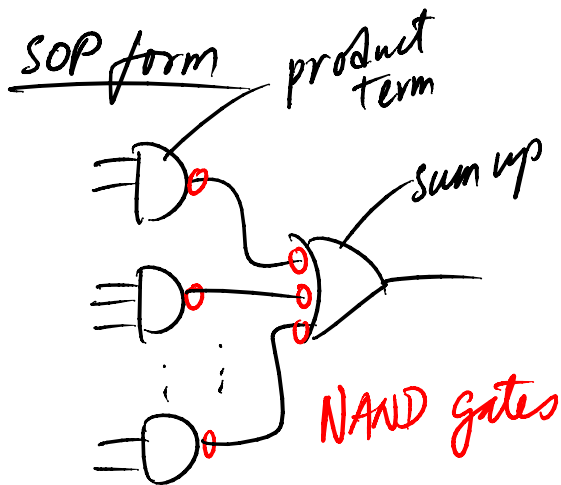
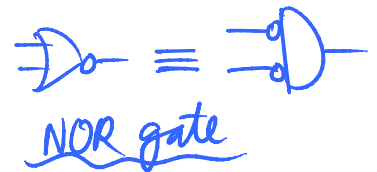


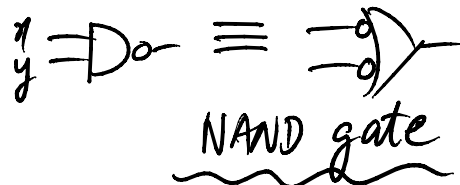
## 2.7 NAND and NOR networks

⇒ Recall de Morgan's rule  $\overline{x} \overline{y} = \overline{x + y}$



$$\overline{x + y} = \overline{x} \cdot \overline{y}$$




POS form ( ) ( )

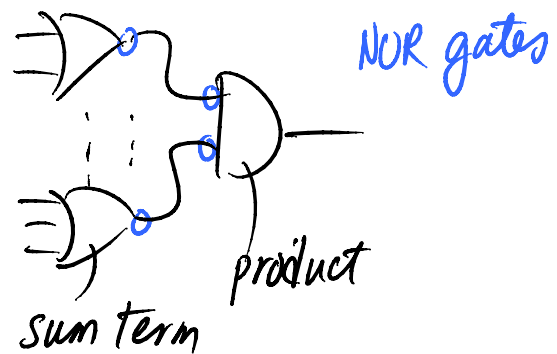

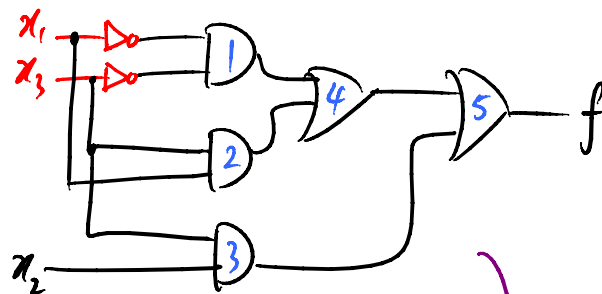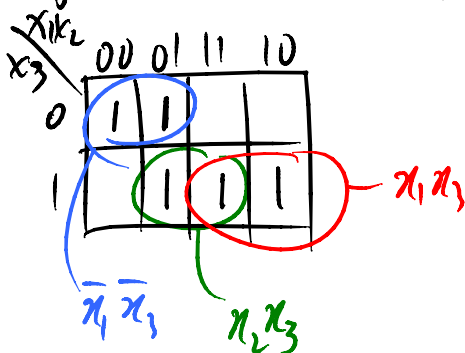example draw cct. diagram using only 2-input NOR gates for  $f = \overline{x_1}x_2 + x_1x_3 + \overline{x_1}\overline{x_3}$  (use as few gates as possible)





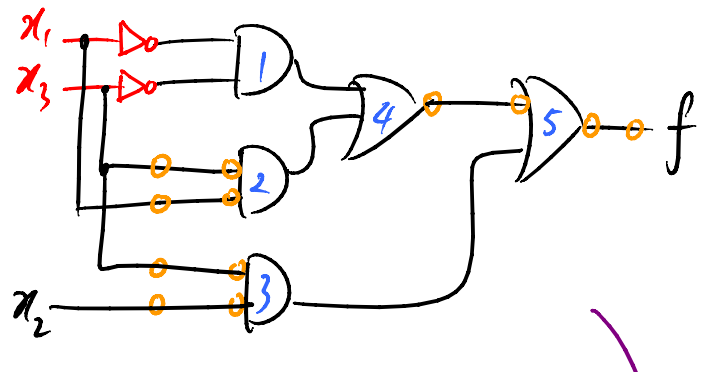make each gate looking like either  $\text{D} \circ$  or  $\text{D} \rangle$



alternative
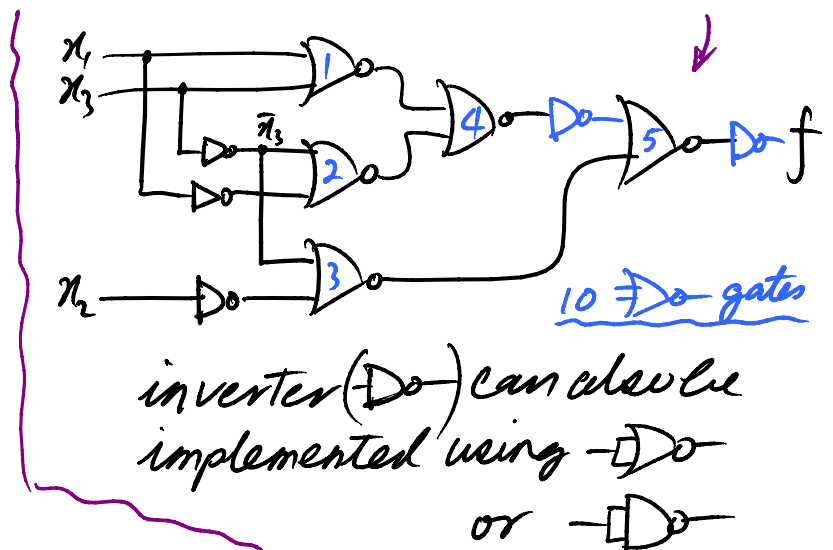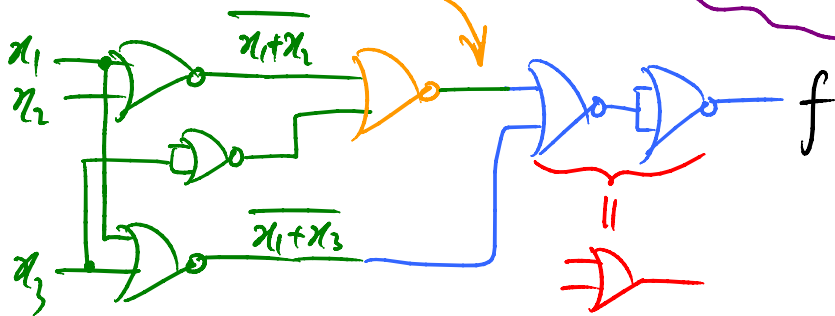
$$\begin{aligned}
 f &= x_1 x_3 + x_2 x_3 + \bar{x}_1 \bar{x}_3 \\
 &= \overline{(x_1 + x_2)} x_3 + \bar{x}_1 \bar{x}_3 \\
 &= \overline{x_1 + x_2 + x_3} + \overline{x_1 + x_3}
 \end{aligned}$$





POS form

$x_1, x_2$	00	01	11	10
$x_3$				
0			0	0
1	0			

$(\bar{x}_1 + x_3)$

$(x_1 + x_2 + \bar{x}_3)$
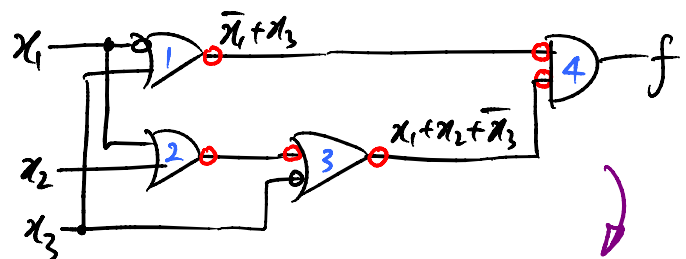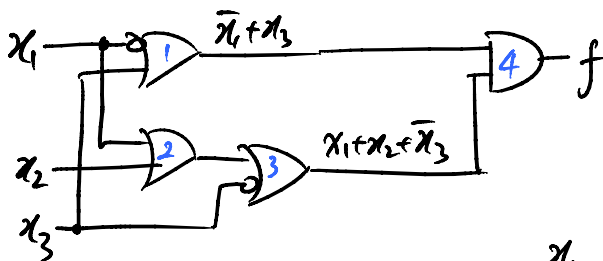
$$f = (\bar{x}_1 + x_3)(x_1 + x_2 + \bar{x}_3)$$



Total # of gates is 7

