
 


### 3.2-3 Adder + Subtractor

recall a full adder circuit

 

Cin	b	a	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1




\* Ai will work as well

Verilog code for a FA: `module FA (input Cin, a, b, output Cout, S);`

conditional assignment `assign S = Cin ^ a ^ b;`  
`if (a == b, Cout = b`  
`else Cout = Cin`  
`endmodule`

Verilog code using a "For" loop

⇒ n-bit ripple-carry adder

 

the "+" operator

$\{C[k+1], S[k]\} = A[k] + B[k] + C[k]$

```
module Add_n(Cin, A, B, Cout, S);
    parameter n=4;
    // A, B, S are [n-1, 0] vectors
    reg [0:n] C;
    always@(*)
    begin
        C[0] = Cin;
        for (k=0; k<n; k=k+1)
        begin
            S[k] = A[k] ^ B[k] ^ C[k];
            C[k+1] = (A[k] == B[k]) ? A[k] : C[k];
        end
        Cout = C[n];
    end
endmodule
```

The "+" operator used on multi-bit vectors

```
module Add_n(Cin, A, B, Cout, S);
    parameter n=4;
    // A, B, S are [n-1, 0] vectors
    always@(*)
    {Cout, S} = A + B + Cin;
endmodule
```

### 3.3 Signed numbers (2's complement)

e.g.  $5 + 1 = 6$

$5 - 1 = 4$

$(0101) + (1111) = (0100)$

$5 - 2 = 3$

$(0101) + (1110) = (0011)$

$\left. \begin{array}{l} -1 \rightarrow 1111 \end{array} \right\}$

$\left. \begin{array}{l} -2 \rightarrow 1110 \end{array} \right\}$

4-bit binary

0	0	0	0	0
+1	0	0	0	1
+2	0	0	1	0
+3	0	0	1	1
+4	0	1	0	0
+5	0	1	0	1
+6	0	1	1	0
+7	0	1	1	1
-8	1	0	0	0
-7	1	0	0	1
-6	1	0	1	0
-5	1	0	1	1
-4	1	1	0	0
-3	1	1	0	1
-2	1	1	1	0
-1	1	1	1	1

4 bits signed #:  $-8 \rightarrow +7$

n bits signed #:  $-2^{n-1} \rightarrow 2^{n-1}-1$

4 bits, to represent  $-k$  we do

$2^4 - k$  eg. find 2's comp. of -3

$\begin{array}{r} 10000 \leftarrow 2^4 \\ -00011 \leftarrow -3 \\ \hline 01101 \end{array}$

not easy to do

Let's do this instead:

$2^4 - 1 - k + 1 = \begin{array}{r} 1111 \leftarrow 2^4 - 1 \\ -0011 \leftarrow -3 \\ \hline 1100 \end{array}$

easy to work with

$+0001 \leftarrow +1$

$1101 \leftarrow 2\text{'s complement of } -3 \text{ using 4-bits}$

2's complement

all -ve # have "1" as the msb.

Short-cut to find 2's comp

eg. 4-bits, we want to represent -6

$+6 \quad 0110$

$1010$

-6 in 2's comp.

→ going from right (LSB) to left (MSB)

→ copy down all "0's and the 1st "1" that you see

→ complement the remaining bits.

Let's make an adder into  
a adder/subtractor

$$A - B \Rightarrow A + (-B)$$

2's comp of -B

This is how we can find the  
2's comp of -B

use an example  
where B is 3

in general

$$\begin{array}{r} 2^4 - 1 \rightarrow | | | | \\ - 3 \quad - 0 0 1 1 \\ \hline \end{array}$$


(This result is in fact the  
complemented value of 3)

$$\rightarrow \begin{array}{r} | | 0 0 \\ + 1 \quad + 0 0 0 1 \\ \hline \end{array} \leftarrow \text{Step 1: } \bar{B}$$

$$\leftarrow \text{Step 2: } +1$$

(This is the 2's comp.  
representation of -3)

$$\rightarrow \begin{array}{r} | | 0 1 \\ \hline \end{array} \leftarrow \text{the result is 2's comp. of -B}$$

 

When performing addition,  $C_{in}$  is set to 0, outputs of  $\oplus$  are  $b_{n-1} \dots b_0$  hence  $A+B$  is performed.

When performing subtraction,  $C_{in}$  is set to 1, outputs of  $\oplus$  will be  $\bar{b}_{n-1} \dots \bar{b}_0$ , hence  $A + (2's \text{ comp of } -B) = A - B$  is performed.