

 
 


 ⇒ What happens if there is either a setup time or hold time violation
meta stable not certain whether its "1" or "0"



7.8.3 Synchronizer





50 MHz, \rightarrow 20ns period

 

(assuming 20ns is long enough for the signal to settle on either "1" or "0")

    
7.8.4 Switch debouncing

SW closing means $V_f = 0V$ (logic 0)
 SW opening means $V_f = V_{DD}$ (logic 1)



charging of capacitor when SW is opened ($V_f = 0$)
 discharging when SW is closed. ($V_f = 1$)

buffer \rightarrow 

 

- charging speed depends on RC value
- discharging quite fast because of low resistance of the closed SW

\rightarrow Using FSM to wait out $\sim ms$

